
# Coplanar waveguide resonators

Mahmoud Almansouri

#### Outline and outcomes

- Superconducting Quantum circuits
- Resonator's noise sources
- Design parameters to consider
- Input-output coupling
- Worked examples
- Full design workflow
- Use cases

#### Superconducting quantum circuit

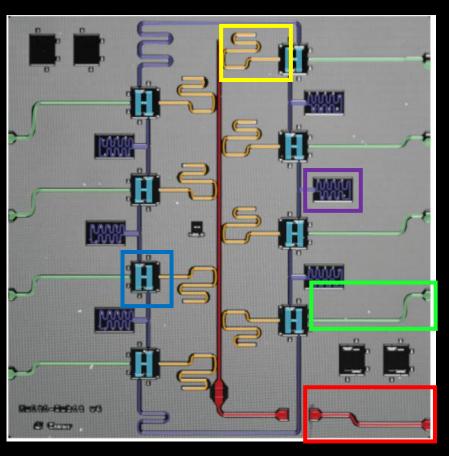

Main components:

1.Resonator CPWr.

2. Qubit (nonlinear inductor).

Complementary:

- 3. Coupler for entanglement CPWr.
- 4. Drive line CPWr.
- 5. Readout line CPWr.

- Resonators are used in quantum circuits for:
  - Entanglement (qbit-qbit coupling).
  - Readout filtering and readout channel.
  - Control and drive of qubit states.
- Therefore, better resonators means less noise in the circuit.

#### What is resonator's loss or noise?

$$Q = \frac{Energy stored}{Energy lost per cycle}$$

#### Internal losses (Qi):

Physical loss sources causes the stored energy in the resonator to dissipate. This is measured assuming the resonator is in complete isolation from all other circuit components.


- Fabrication defects
- Metal contamination
- Substrate loss tangent

#### External losses (Qe):

Simulated loss is determined by capacitive or inductive coupling between the circuit components using a simulation software.

- Crosstalk between circuit elements.
- Strong coupling between drive lines or readout line.

#### Design parameters in resonators

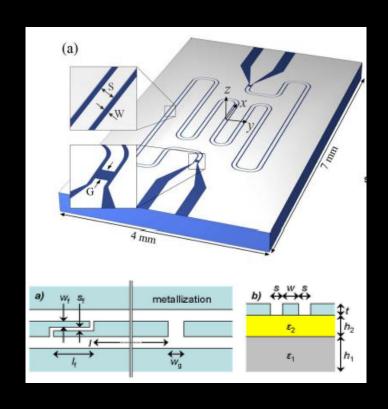

- Frequency:  $f = \frac{c}{\sqrt{\epsilon_{eff}}} \frac{1}{2l}$  or  $f = \frac{c}{\sqrt{\epsilon_{eff}}} \frac{1}{4l}$
- Characteristic impedance:  $Z_o = \sqrt{\frac{L_l}{C_l}}$
- External quality factor (Qe)
- Capacitance and coupling.

- HFSS
- CST
- COMSOL


Where:

$$L_l = \frac{\mu_0}{4} \frac{K(k'_0)}{K(k_0)}$$
 and  $C_l = 4\varepsilon_0 \varepsilon_{eff} \frac{K(k_0)}{K(k'_0)}$ 

$$k_0 = \frac{w}{w + 2s}$$
 and  $k'_0 = \sqrt{1 - k_0^2}$ 


Typically W:S is 2:1 (w=20  $\mu m$  and s=10  $\mu m$  ):


### Example of a resonator design

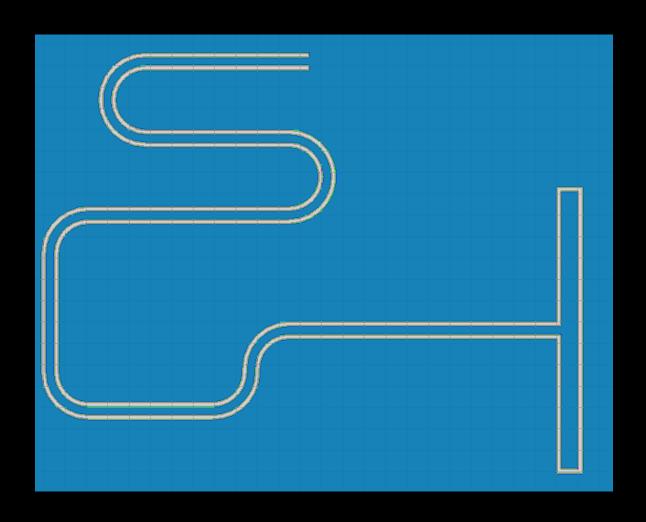


- Middle conductor to gap is 2:1
- Total length corresponds to 6 GHz
- Blue is the metal (Perfect E) and white is silicon.

### Input-output coupling

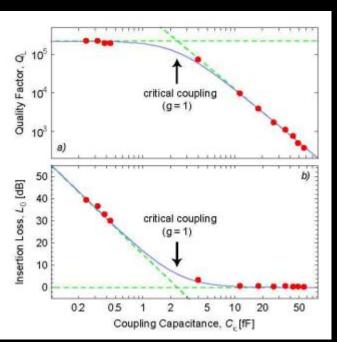


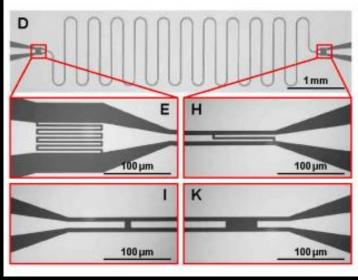

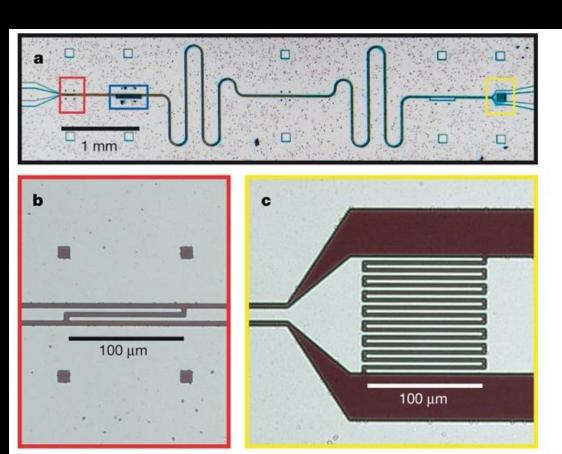
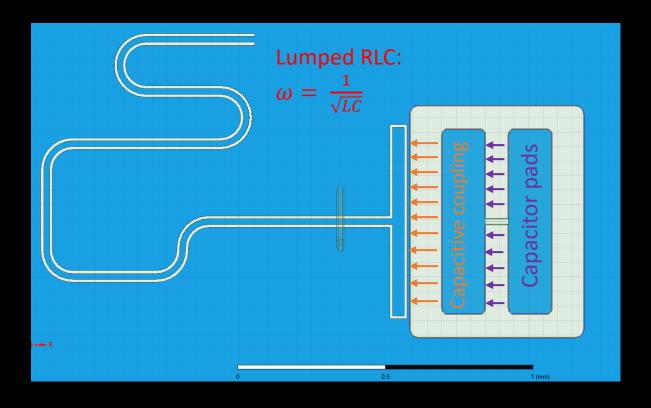
#### More on capacitive coupling

 Capacitive coupling is also important in terms of connecting different circuit elements.




All capacitances are computed with Maxwell 3D including:

- Capacitor pads
- Qubit-resonator coupling
- Resonator-readout coupling
- Qubit-qubit coupling

#### Additionally:

The coupling strength can be estimated from the external quality factor of each component on HFSS.

### Complete design workflow

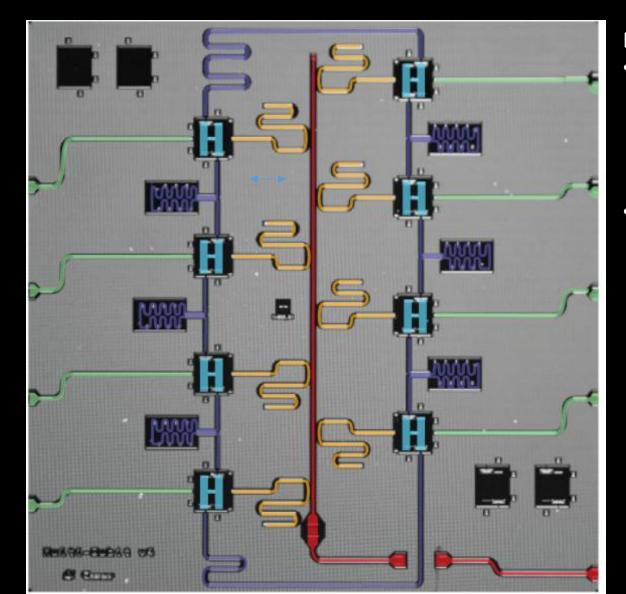

#### Full design steps:

- Draw coplanar structures for all resonators and readout lines:
  - Adjust the frequencies based on length
  - Adjust the impedance matching (2:1)
  - Adjust the external Q
- Qubit pads:
  - Optimize the capacitance with Maxwell 3D to get the qubit frequency
  - Reach the desired coupling by optimizing Qe and capacitance.
  - Apply lumped RLC ~12 nH box to simulate the frequency classically.
    - For accurate frequency and anharmonicity use PyEPR instead.

#### Discussion:use cases

- Algorithm specific design
- High kinetic inductance
- Compact fields and resonators
- Remote entanglement


All of the above are based on the design principles we discussed.

### Thanks


Questions?

## Design geometry and field intensity can also change Qi


Spiral geometry (10M Qi)

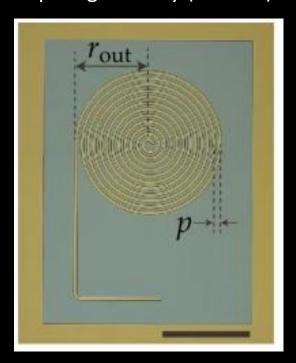

Spiral geometry (100K Qi)

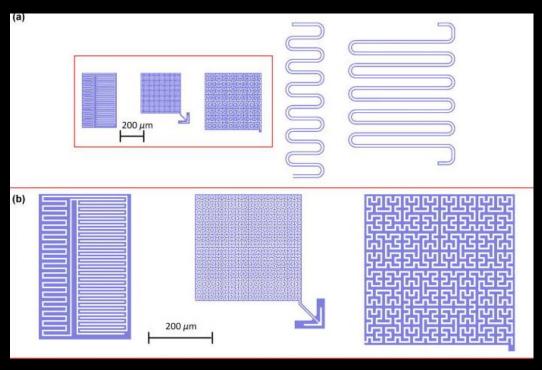

CPW geometry (2-6M Qi)

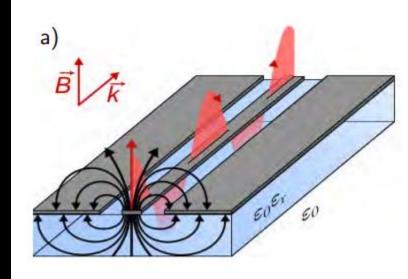

### Example on how to design resonators on HFSS

